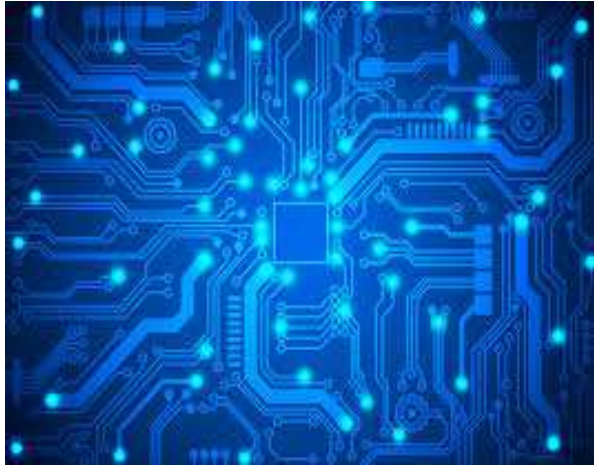


Digital Systems: Boolean Algebra and Logic Gates




DEFINITION:

Boolean Algebra is the algebra of truth values and operations performing on them which is used in Digital Circuits for performing logical operations.

Boolean Constants and Variables

- Logical statements can have either two values yes or no, true or false, 0 or 1.
- Boolean 0 and 1 do not represent actual numbers but instead represent the state, or logic level.




Logic 0	Logic 1
False	True
Off	On
Low	High
No	Yes
Open switch	Closed switch

Truth Tables

- A truth table is a means for describing how a logic circuit's output depends on the logic levels present at the circuit's inputs.

Inputs		Output
A	B	x
1	1	1
0	1	0
1	0	0
0	0	0

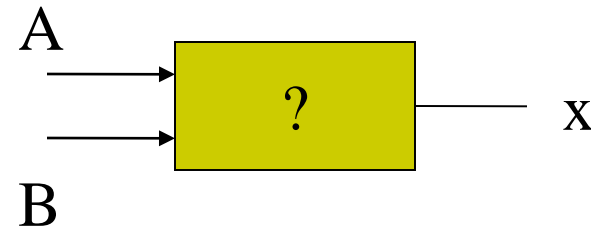

Three Basic Logic Operators

- OR
- AND
- NOT

OR Operation

- Boolean expression for the OR operation:


$$x = A + B$$

- The above expression is read as “x equals A OR B”

OR

A	B	x = A + B
0	0	0
0	1	1
1	0	1
1	1	1

(a)

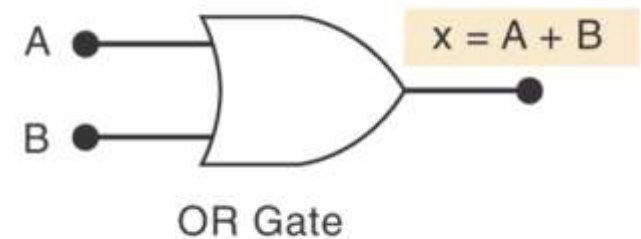

(b)

AND Operation

- Boolean expression for the AND operation:


$$x = A \cdot B$$

- The above expression is read as “x equals A AND B”

AND

A	B	$x = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

(a)

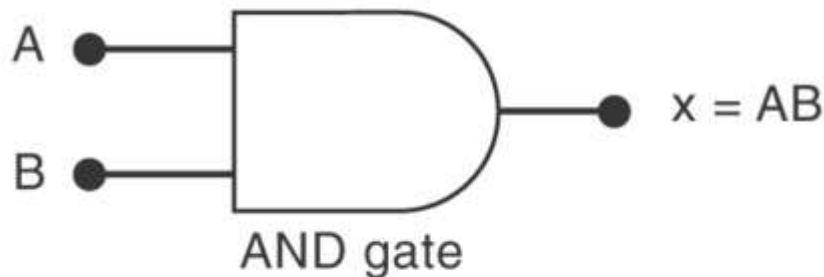



(b)

NOT Operation

- The NOT operation is an unary operation, taking only one input variable.
- Boolean expression for the NOT operation:
 $x = \bar{A}$
- The above expression is read as “x equals the inverse of A”
- Also known as inversion or complementation.
- Can also be expressed as: A'

NOT	
A	x = \bar{A}
0	1
1	0

(a)

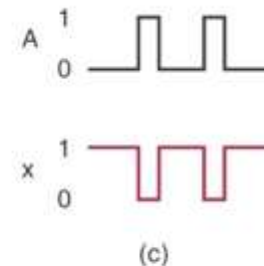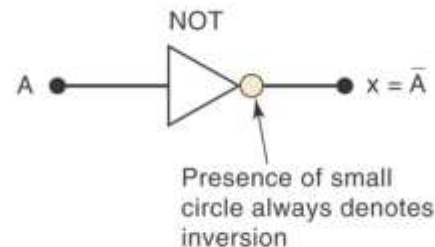


LOGIC GATES

- OR
- AND
- NOT
- NAND
- NOR

OR Gate

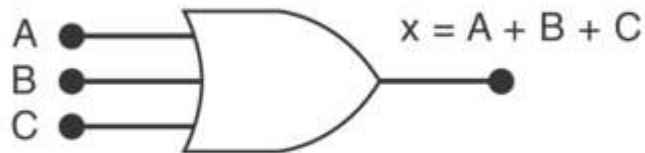- An OR gate is a gate that has two or more inputs and whose output is equal to the OR combination of the inputs.




A	B	C	$x = A + B + C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

AND Gate

- An AND gate is a gate that has two or more inputs and whose output is equal to the AND product of the inputs.

A	B	C	$x = ABC$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

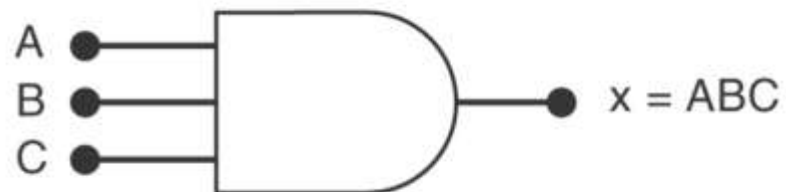


NOT Gate


The symbol and Truth Table for NOT gate is given below:

NOT	
A	$x = \bar{A}$
0	1
1	0

(a)

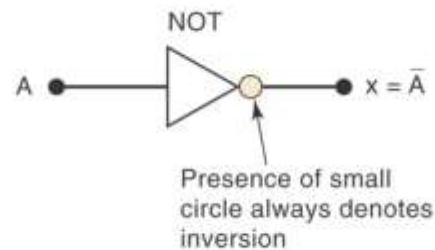

(b)

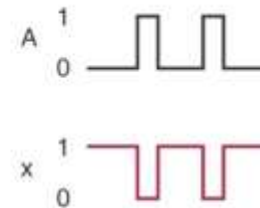


(c)

A


Describing Logic Circuits Algebraically

- Any logic circuits can be built from the three basic building blocks: OR, AND, NOT
- Example 1: $x = A B + C$
- Example 2: $x = (A+B)C$
- Example 3: $x = \overline{(A+B)}$

Examples 1,2

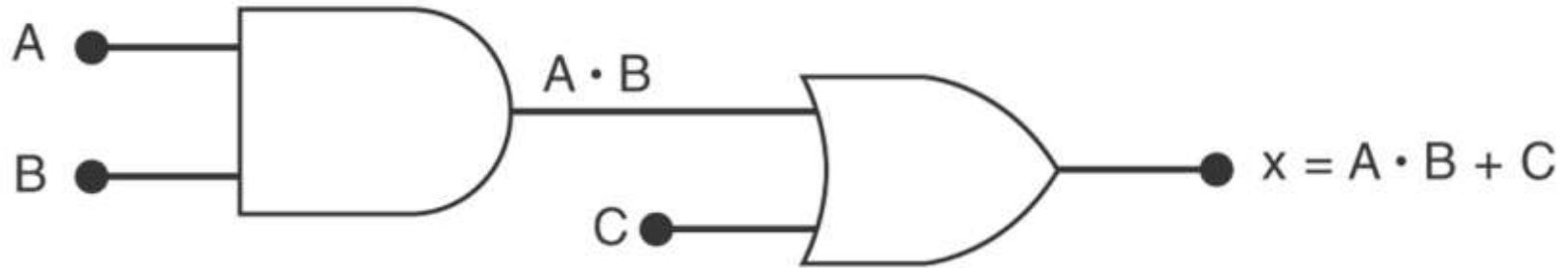


(a)

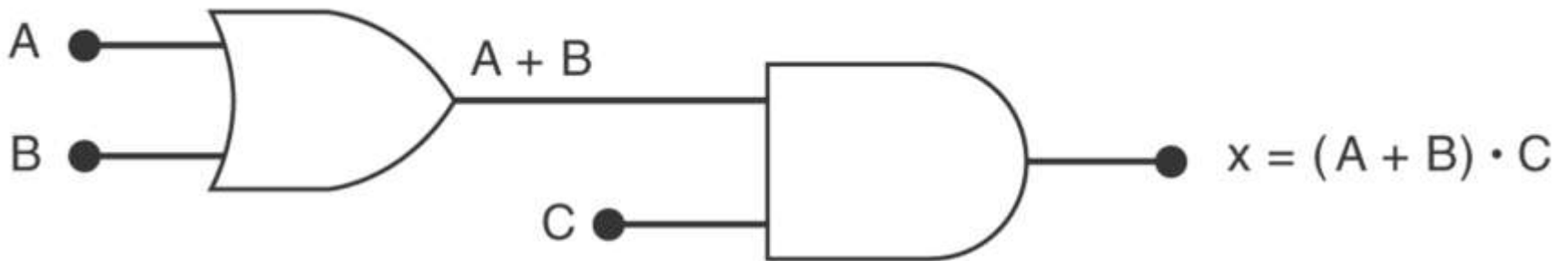


(b)

Examples 3

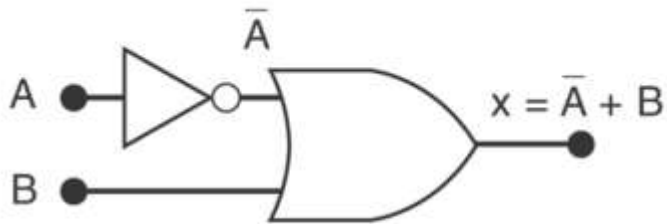

(a)

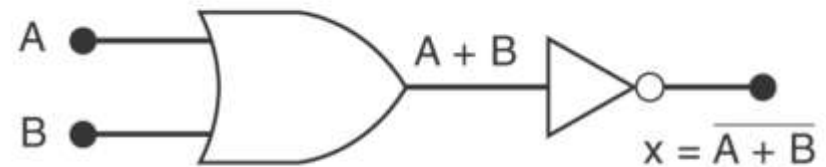


(b)

Evaluating Logic-Circuit Outputs

- $x = \overline{A}BC(\overline{A+D})$
- Determine the output x given A=0, B=1, C=1, D=1.
- Can also determine output level from a diagram

Examples

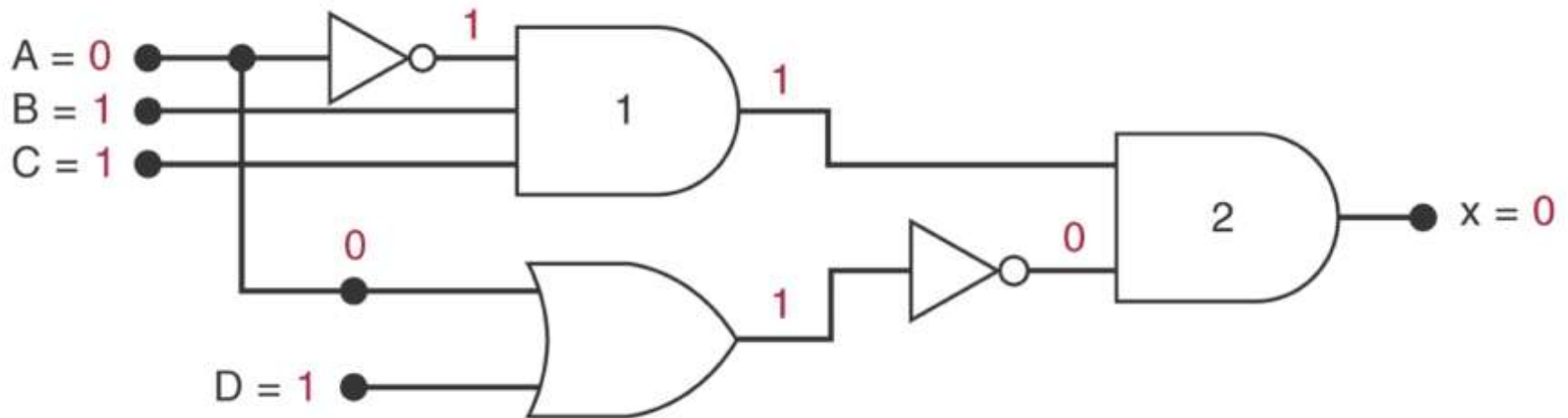


Draw the Logic Gate:

- $AB + C'D$
- $A(B + C') + B'D'$
- $A' [(B + C)' + AB]$

Draw the Truth Table:


- $AB + (BC)'$
- $A(B' + C') + BC'$
- $X' [(Y + Z)' + XY]$

Derive the Boolean Expression

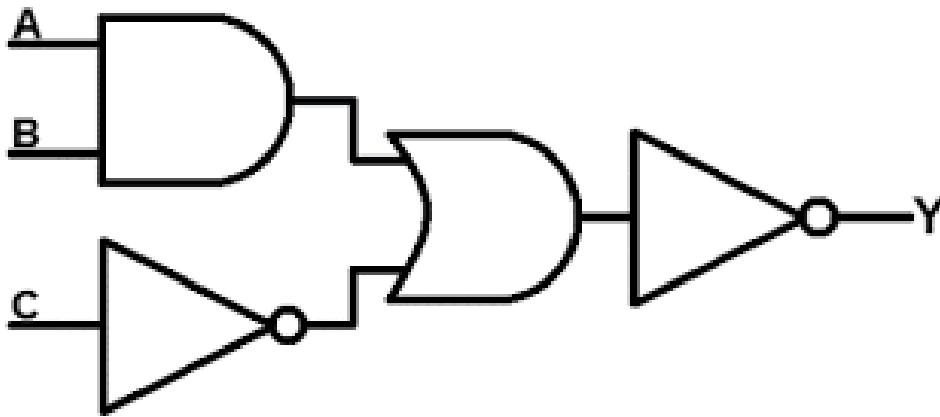

NAND Gate

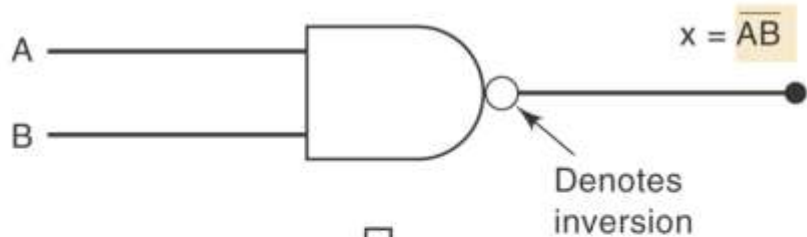- Boolean expression for the NAND operation:
 $x = \overline{A B}$



(a) ↓



(b)


A	B	AND	NAND
		AB	\overline{AB}
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

(c)

NOR Gate

- Boolean expression for the NOR operation:

$$x = \overline{A + B}$$

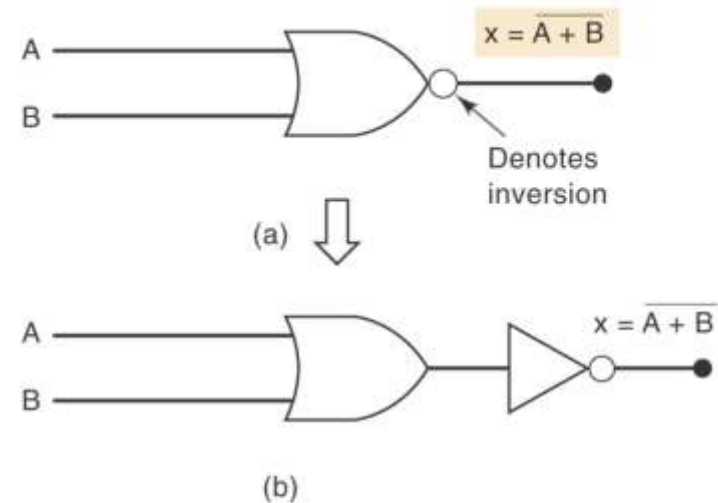


A	B	OR		NOR	
		A + B		$\overline{A + B}$	
0	0	0		1	
0	1	1		0	
1	0	1		0	
1	1	1		0	

(c)

Boolean Theorems and Laws

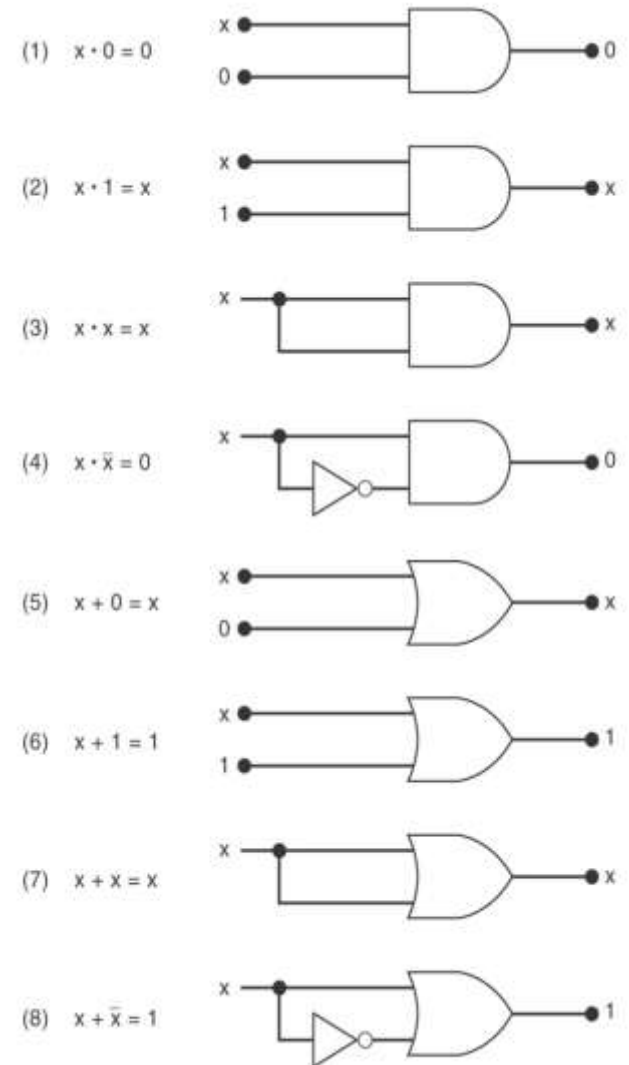- $x * 0 = 0$ Fallacy
- $x + 1 = 1$ Tautology
- $x * x = x$ Idempotence Law
- $x + x = x$ Idempotence Law
- $x * x' = 0$ Complementarity Law
- $x + x' = 1$ Complementarity Law
- $x'' = x$ Involution Law
- $x + 0 = x$
- $x * 1 = x$



Boolean Theorems and Laws

- $x+y = y+x$ // Commutative Law
- $x*y = y*x$
- $x+(y+z) = (x+y)+z = x+y+z$ // Associative Law
- $x(yz) = (xy)z = xyz$
- $x(y+z) = xy+xz$ // Distributive Law
- $(w+x)(y+z) = wy+xy+wz+xz$
- $x+xy = x$ // Absorption Law


Prove it by Truth Table

De'Morgan's Theorems


(Break the line change the sign)

- $(x+y)'=x'y'$
- Implications and alternative symbol for NOR function
- $(xy)'=x'+y'$
- Implications and alternative symbol for NAND function
- Process of Demorganization:
 - (i) Complement entire function
 - (ii) Change all AND to OR and all OR to AND
 - (iii) Complement each of the individual variables

Demorgan's Theorem

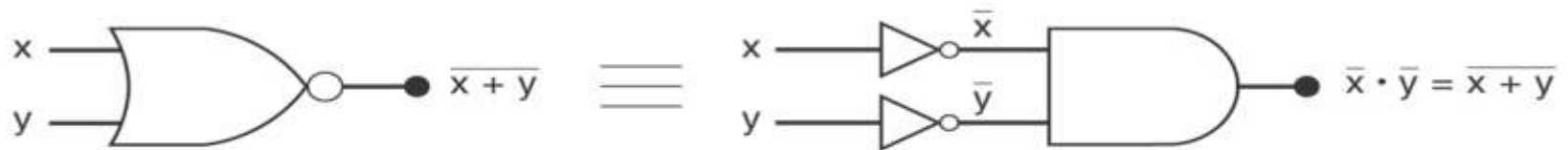


(a)

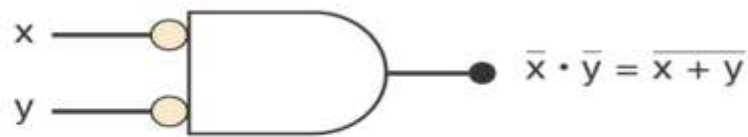


(b)

Demorgan's Theorem

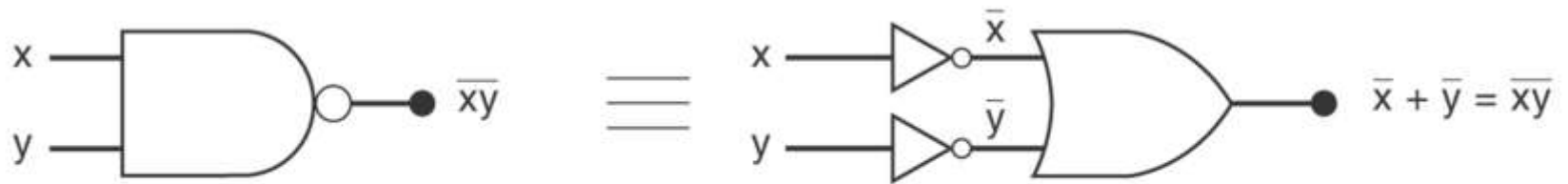


(a)

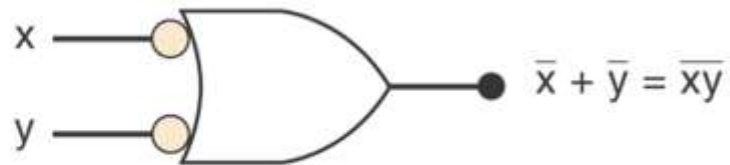

(b)

Universality of NAND Gates

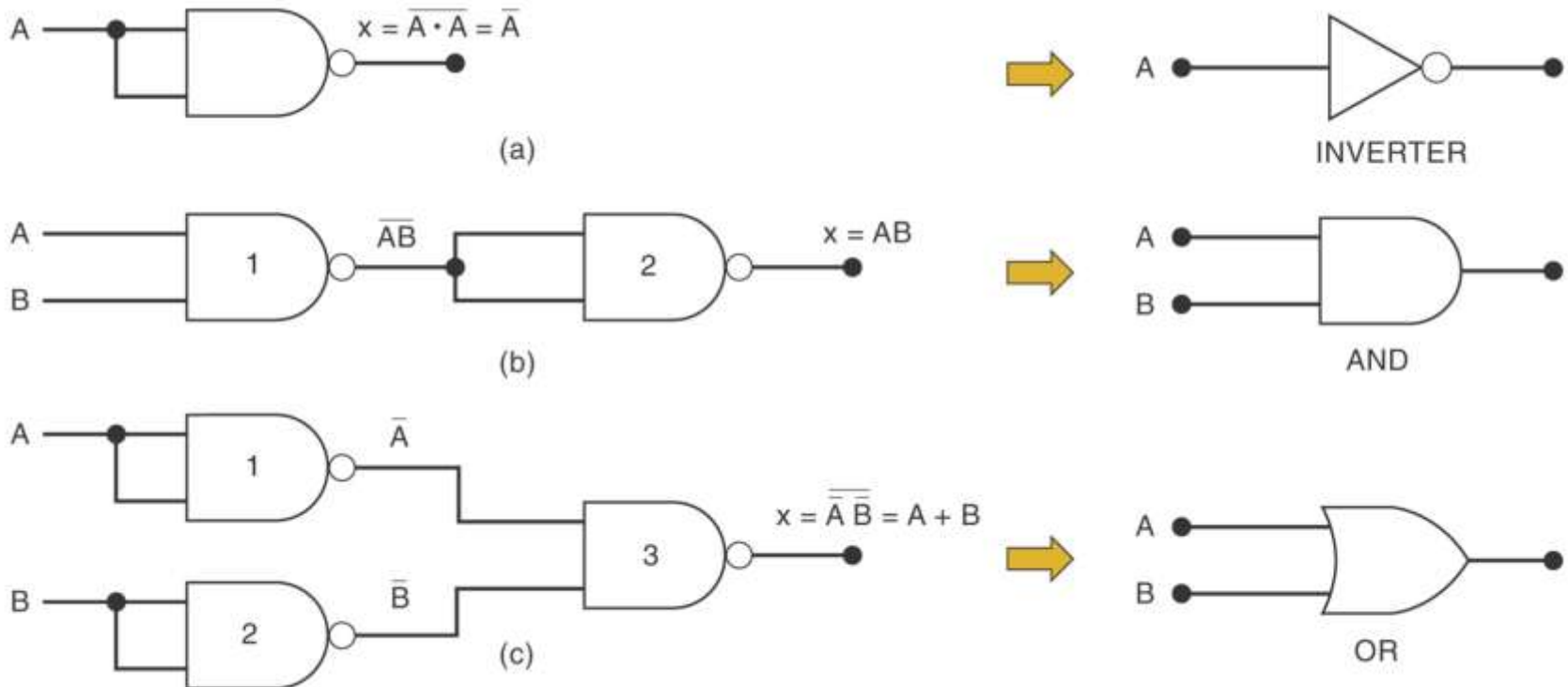

Universality of NOR Gates

